

**III B. Tech I Semester Regular Examinations, February-2022**  
**LINEAR IC APPLICATIONS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any **FIVE** Questions **ONE** Question from **Each unit**

All Questions Carry Equal Marks

\*\*\*\*\*

**UNIT-I**

1. a) Name the most important parameters of an operational amplifier. [6M]  
What are their ideal values and practical values?
- b) Explain the terms input offset current, input offset voltage and PSRR with respect to an Op-Amp. [9M]

**(OR)**

2. a) For a given Op-Amp, CMMR =  $10^5$  and differential gain  $A_d = 10^5$ . [9M]  
Determine the common-mode gain  $A_{cm}$  of the Op-Amp.
- b) What are the differences between compensated and uncompensated Op-Amp? Explain. [6M]

**UNIT-II**

3. a) Derive the expression for gain of a non-inverting Op-Amp amplifier. [7M]
- b) With a neat sketch explain the operation of Anti log Amplifiers and derive the expression for its output voltage. [8M]

**(OR)**

4. a) Using three Op-Amps draw the circuit diagram of an instrumentation amplifier and derive the expression for its output voltage. [8M]
- b) Draw the circuit diagram of a practical log amplifier and obtain an expression for its output voltage. [7M]

**UNIT-III**


5. a) Design a first order high pass filter with a cutoff frequency of 1 kHz and pass band gain of 11. Also draw its frequency response. [8M]
- b) Explain the operation of IC 1496 balanced modulator with a neat diagram. [7M]

**(OR)**

6. a) Design a wide band-pass filter with  $f_H = 200\text{Hz}$ ,  $f_L = 1\text{ kHz}$  and a pass-band gain = 4. Draw the frequency response and calculate Q factor for the filter. [8M]
- b) Describe any two applications of four quadrant multiplier. [7M]

**UNIT-IV**

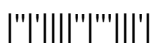7. a) Design a symmetrical square wave generator with 1 kHz frequency and 5V peak value using 555 timer IC. Assume necessary data. [8M]
- b) Explain the lock-in range and capture range of a PLL. [7M]



(OR)

8. a) Using 555 timer, design a monostable multivibrator to produce pulses of width of 110 msec. Use a 1  $\mu$ F capacitor. [8M]  
b) With a neat sketch, explain IC 566 VCO operation and discuss any two applications. [7M]

UNIT-V

9. a) Draw the circuit of weighted resistor DAC and derive expression for output-analog voltage. [8M]  
b) Draw the simplified block diagram of a successive approximation ADC and explain its working. [7M]

(OR)

10. a) With a clear block diagram explain the data conversion procedure for dual slope ADC. [8M]  
b) Draw the circuit of a ladder type DAC for 4 bits and derive expression for the output voltage. [7M]

\*\*\*\*\*

