

III B. Tech I Semester Regular Examinations, February-2022
LINEAR INTEGRATED CIRCUITS AND APPLICATIONS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 75

Answer any **FIVE** Questions **ONE** Question from **Each unit**
 All Questions Carry Equal Marks

UNIT-I



1. a) Explain the operation of an improved version of current mirror circuit with a neat circuit diagram. [8M]
 - b) Design a regulated power supply using three-terminal IC to give $V_o = +5$ V, $I_o = 0.6$ A, $V_i = 12$ V_{DC}, $T_A = 60^\circ\text{C}$. [7M]
- (OR)**
2. a) Explain the operation of dual input balanced output differential amplifier (ac equivalent) and derive the expressions for input resistance and output resistance. [8M]
 - b) For an Op-amp, PSRR is 70 dB, CMRR is 10^5 , and differential mode gain is 10^5 . The output voltage changes by 20 V in 4 μs . Calculate: [7M]
 - i) Common mode gain
 - ii) Slew rate.

UNIT-II


3. a) Draw the circuit diagram of a logarithmic amplifier using Op-Amps and explain its operation. [8M]
 - b) Design an Op-amp based circuit to produce an output $-(V_1 + 2V_2 - 5V_3)$, where V_1 , V_2 and V_3 are the input voltages. [7M]
- (OR)**
4. a) With a circuit diagram explain the working of a current to voltage converter. [8M]
 - b) What are the differences between conventional rectifier and precision rectifier? Draw the circuit diagram of a full-wave precision rectifier using Op-amp. [7M]

UNIT-III

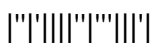 5. a) Consider the Op-amp high pass filter with 20 dB/decade roll-off shown below figure. Calculate the value of R if $C = 0.001$ μF and $f_c = 15$ kHz. [8M]



- b) Draw the circuit for first-order lowpass filter and high pass filter and derive the expressions for cut-off frequencies. [7M]
- (OR)**
6. a) Give the design procedure for 60 dB/decade high pass filter in Butterworth configuration when the desired cut-off frequency is 200 Hz. [8M]
- b) For the circuit shown, determine the values of R_1 and R_2 to get a cut-off frequency of 5 kHz. Assume $C_1 = 0.01 \mu\text{F}$. [7M]

 **UNIT-IV**

7. a) Design a 555 astable multivibrator to operate at 10 kHz with 40% duty cycle. Assume necessary data. [8M]
- b) Draw the circuit of a 565 PLL IC and explain its working. [7M]
- (OR)**
8. a) Design a square-wave generator using 555 timer for a frequency of 150 Hz and 70% duty cycle. Assume $C = 0.1 \text{ mF}$. [8M]
- b) How a phase locked loop is used as a FM demodulator? Explain with a neat diagram. [7M]

UNIT-V

9. a) Explain the counter type ADC with a neat block diagram and list out its disadvantages. [8M]
- b) A 4-bit R-2R ladder type D/A converter having resistor values of $R = 10 \text{ k}\Omega$ and $2R = 20 \text{ k}\Omega$, uses V_R of 10V. Find: i) the resolution of the D/A converter, and ii) I_o for a digital input of 1101. [7M]
- (OR)**
10. a) Explain the working of dual slope-type of ADC with a neat diagram. [8M]
- b) Explain the principle of inverted R-2R type DAC and write its advantages and disadvantages. [7M]

